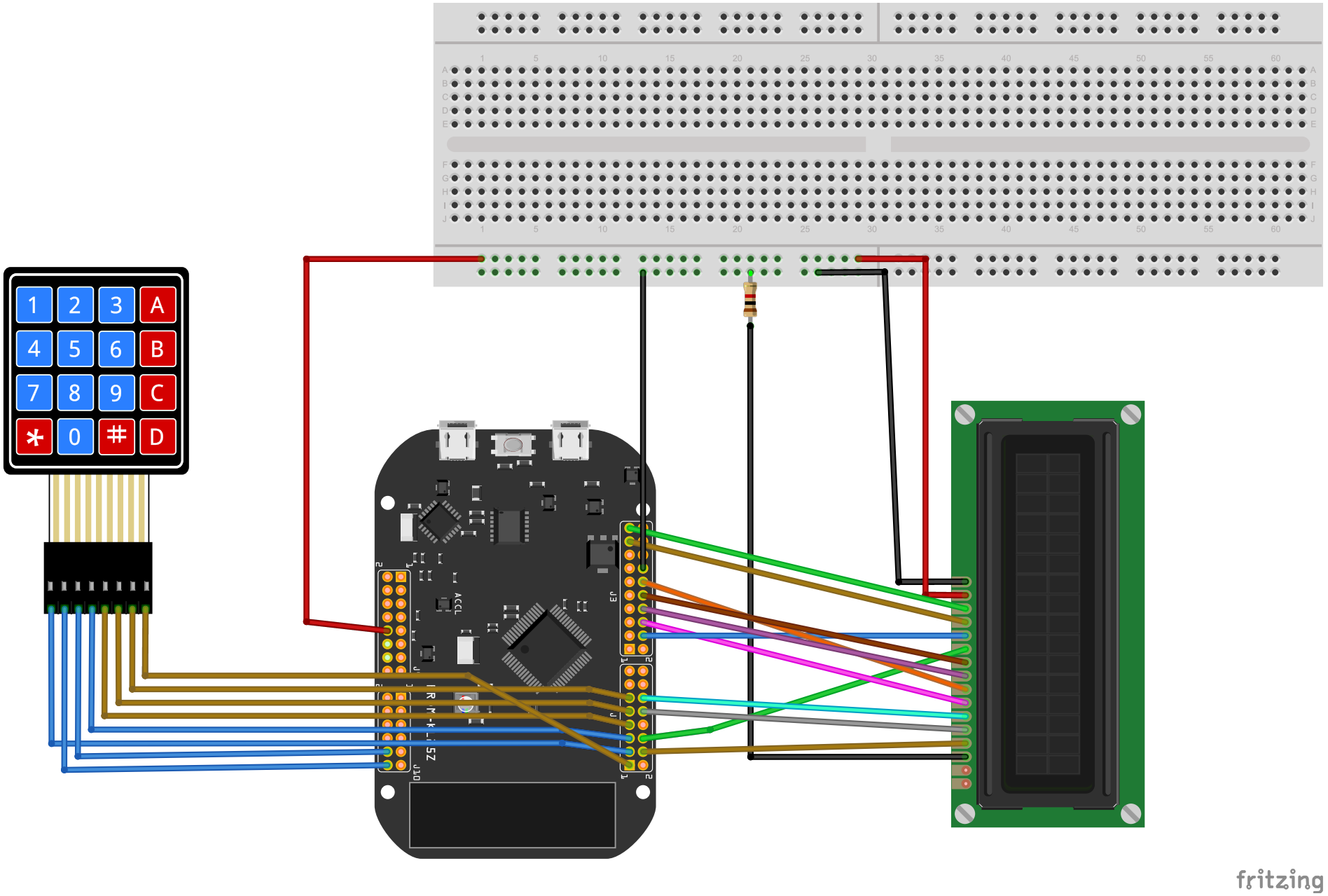
1 2 3 A
4 5 6 B
7 8 9 C
* 0 # D
fritzing

Since we are not using Arduino Headers, cable positions are bit messy.

fritzing